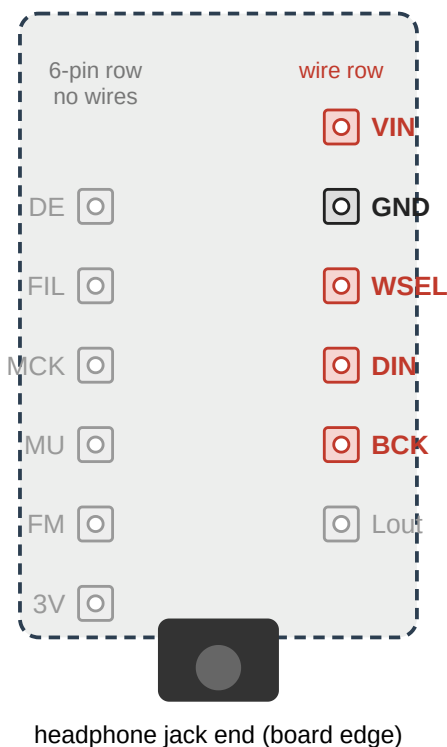


Pod: DAC wiring


Taken from Adafruit's own board files, matched to your photos. Turn the board over so the **headphone jack end points towards you**: the row of 6 pins on the **left** needs no wires; the row on the **right** has the 5 pins that do.

DAC pins, seen from the solder side




Where each wire goes on the Pico

Row starting at pin 40 (USB end) →

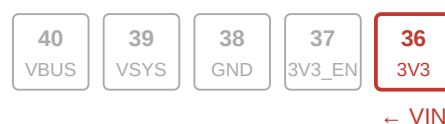

Last 4 pins of the GP0 row (antenna end)

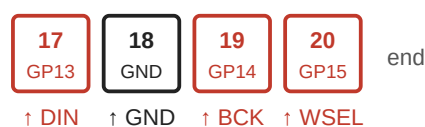

The 5 wires

- 1. DAC VIN → Pico pin 36 (3V3)**
5th pin from the USB end, row with pin 40
- 2. DAC GND → Pico pin 18 (GND)**
3rd pin from the antenna end, GP0 row
- 3. DAC WSEL → Pico pin 20 (GP15)**
last pin at the antenna end, GP0 row
- 4. DAC DIN → Pico pin 17 (GP13)**
4th pin from the antenna end, GP0 row
- 5. DAC BCK → Pico pin 19 (GP14)**
2nd pin from the antenna end, GP0 row

Before soldering: one 10-second check

- Multimeter on continuity (beep). One probe on the **second pin from the top** of the right-hand row.
- Other probe on the outer metal tab of the headphone jack. It must **beep**: that pin is GND, so the row is the right way round.
- If it doesn't beep, stop and send me a photo before wiring.

Tips

- Cut the bent pins down to about 2 mm, then solder each one to its own pad only. Bent pins lying across neighbouring pads can short.
- Solder the six left-row pins and Lout too (for strength), but connect nothing to them. The **3V** pin especially must stay unconnected.
- These Pico pins match the current firmware (pod.uf2): DIN = GP13, BCK = GP14, WSEL = GP15.